

# Vp250 Problem Set 5

Runxi Wang 519021911166

## Problem 1

- (a) For two resistors in series, the equivalent resistance is  $R = R_1 + R_2$ .

Since  $R_1 = \rho_1 \frac{L}{A} = \rho_{01}(1 + \alpha_1(T - T_0)) \frac{L}{A}$ ,  
and  $R_2 = \rho_2 \frac{L}{A} = \rho_{02}(1 + \alpha_2(T - T_0)) \frac{L}{A}$ ,  
we can get

$$\begin{aligned} R &= \frac{L}{A} [\rho_{01} + \rho_{02} + (\rho_{01}\alpha_1 + \rho_{02}\alpha_2)(T - T_0)] \\ &= \frac{L}{A} (\rho_{01} + \rho_{02}) \left[ 1 + \frac{\rho_{01}\alpha_1 + \rho_{02}\alpha_2}{\rho_{01} + \rho_{02}} (T - T_0) \right] \end{aligned}$$

So the effective temperature coefficient is  $\frac{\rho_{01}\alpha_1 + \rho_{02}\alpha_2}{\rho_{01} + \rho_{02}}$ .

- (b) For two resistors in parallel, the equivalent resistance is  $R = \frac{R_1 R_2}{R_1 + R_2}$ .

Since  $R_1 = \rho_1 \frac{L}{A} = \rho_{01}(1 + \alpha_1(T - T_0)) \frac{L}{A}$ ,  
and  $R_2 = \rho_2 \frac{L}{A} = \rho_{02}(1 + \alpha_2(T - T_0)) \frac{L}{A}$ ,  
we can get

$$\begin{aligned} R &= \frac{L}{A} \cdot \frac{\rho_{01}(1 + \alpha_1(T - T_0)) \cdot \rho_{02}(1 + \alpha_2(T - T_0))}{\rho_{01}(1 + \alpha_1(T - T_0)) + \rho_{02}(1 + \alpha_2(T - T_0))} \\ &= \frac{L}{A} \cdot \frac{\rho_{01}\rho_{02}(1 + \alpha_1\alpha_2(T - T_0)^2 + (\alpha_2 + \alpha_1)(T - T_0))}{\rho_{01} + \rho_{02} + (\rho_{01}\alpha_1 + \rho_{02}\alpha_2)(T - T_0)} \\ &\quad (\text{Take } T_0 = 0) \\ &= \frac{L}{A} \cdot \frac{\rho_{01}\rho_{02}(1 + \alpha_1\alpha_2 T^2 + (\alpha_2 + \alpha_1)T)}{\rho_{01} + \rho_{02} + (\rho_{01}\alpha_1 + \rho_{02}\alpha_2)T} \end{aligned}$$

Differentiate R w.r.t T and insert T=0, we get:

$$R' = \frac{L}{A} \cdot \frac{\rho_{01}\rho_{02}(\alpha_1\rho_{02} + \alpha_2\rho_{01})}{(\rho_{01} + \rho_{02})^2}$$

Since  $R = \frac{L}{2A}\rho_0(1 + \alpha(T - T_0))$ ,  $R' = \frac{L}{2A}\rho\alpha$ . The effective temperature coefficient is

$$\alpha = \frac{R'2A}{\rho_0 L} = \frac{\alpha_1\rho_{02} + \alpha_2\rho_{01}}{\rho_{01} + \rho_{02}}$$

## Problem 2

$$R_{eq} = 20 \parallel (3 + (4 + 6) \parallel (8 \parallel 9)) = \frac{14460}{3143} \approx 4.6\Omega$$

## Problem 3

$$R_{eq} = R \parallel R \parallel R + R \parallel R \parallel R \parallel R \parallel R + R \parallel R \parallel R = \frac{5}{6}R$$

## Problem 4

- (a)

$$I = \frac{\varepsilon_1 - \varepsilon_2}{R + 2r} = \frac{12 - 8}{8 + 2 \cdot 1} = 0.4A$$

direction: downwards

(b)

$$P_R = I^2 R = 0.4^2 \cdot 8 = 1.28W$$
$$P_r = 2I^2 r = 2 \cdot 0.4^2 \cdot 1 = 0.32W$$

Then the total power is:

$$P = P_R + P_r = 1.6W$$

(c) In  $\varepsilon_1$ , rate:

$$P_1 = \varepsilon_1 I = 12 \cdot 0.4 = 4.8W$$

(d) In  $\varepsilon_2$ , rate:

$$P_2 = \varepsilon_2 I = 8 \cdot 0.4 = 3.2W$$

(e) The overall rate of production of electrical energy is 4.8W.

The overall rate of assumption of energy is the combination of the power consumed in  $R$ , two internal resistance and the charged battery. And their sum is  $1.28 + 0.32 + 3.2 = 4.8W$ , which is equal to the production.

## Problem 5

Set the current through  $R_1$  to be  $I_1$  (downwards positive), the current through  $R_2$  to be  $I_2$  (upwards positive), the current through  $R_3$  to be  $I_3$  (leftwards positive).

For the mesh in the left:

$$\varepsilon_1 - I_1 R_1 - \varepsilon_2 - I_2 R_2 = 0$$

For the mesh in the right:

$$\varepsilon_3 - I_3 R_3 + I_2 R_2 = 0$$

By Junction Rule:

$$I_1 = I_2 + I_3$$

Then we get:

$$I_1 = \frac{99}{19}A$$
$$I_2 = -\frac{21}{19}A$$
$$I_3 = \frac{120}{19}A$$


So the current through  $R_1$  is  $\frac{99}{19} = 5.21A$  (direction: downwards)

The current through  $R_2$  is  $\frac{21}{19} = 1.11A$  (downwards).

The current through  $R_3$  is  $\frac{120}{19} = 6.32A$  (leftwards).

## Problem 6

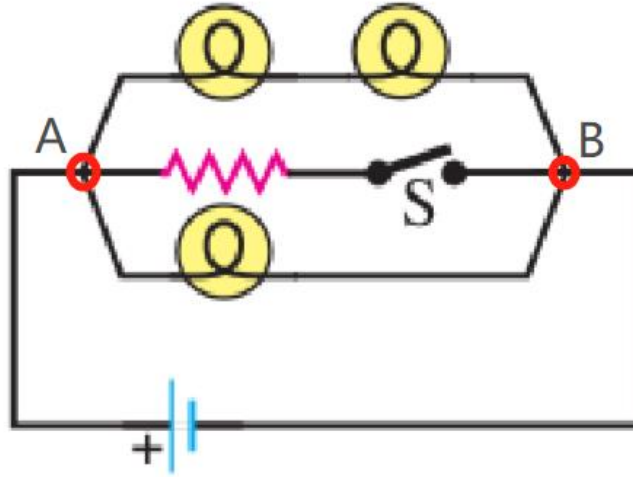(a) No change. Because the voltage between the two node A and B will not change after turning on the switch S. Then the power consumed by the bulb will not change too.



- (b) The brightness of the bulb will be lower.

Because when the switch is turned on, the equivalent resistance between node A and B has  $\frac{1}{R} = \frac{1}{R_{\text{additional}}} + \frac{1}{R_{\text{original}}}$ . But the resistance before turning on the switch has  $\frac{1}{R} = \frac{1}{R_{\text{original}}}$ . We can see that  $\frac{1}{R}$  becomes larger and so  $R$  becomes smaller, which means the voltage between A and B drops. So the power consumed by the bulb is lower.

## Problem 7

Set the current through  $\varepsilon$  as  $I$ . When the galvanometer reads 0, the current through P and X is:

$$I_{PX} = I \frac{M + N}{M + N + P + X}$$

The current through M and N is:

$$I_{MN} = I \frac{P + X}{M + N + P + X}$$

By loop rule:

$$I_{PX}P = I_{MN}N$$

So we get

$$\begin{aligned} IP \frac{M + N}{M + N + P + X} &= IN \frac{P + X}{M + N + P + X} \\ \Rightarrow P(M + N) &= N(P + X) \Rightarrow X = \frac{PM}{N} \end{aligned}$$

## Problem 8

- (a)

$$q(t) = 7 \cdot 10^{-6} e^{-\frac{t_d}{670 \cdot 10^3 \cdot 0.92 \cdot 10^{-6}}} = 1.6 \cdot 10^{-19} \Rightarrow t_d = 19.36s$$

- (b) Yes.

$$q(t) = Q_{\text{max}} e^{-\frac{t_d}{RC}} = e \Rightarrow -\frac{t_d}{RC} = \ln \frac{e}{Q_{\text{max}}} \Rightarrow t_d = -RC \ln \frac{e}{Q_{\text{max}}}$$

The time constant is  $RC$ .  $\ln \frac{e}{Q_{\text{max}}}$  is a constant for given  $Q_{\text{max}}$ . So the time required to reach this state always the same number of time constants, independent of R and C.