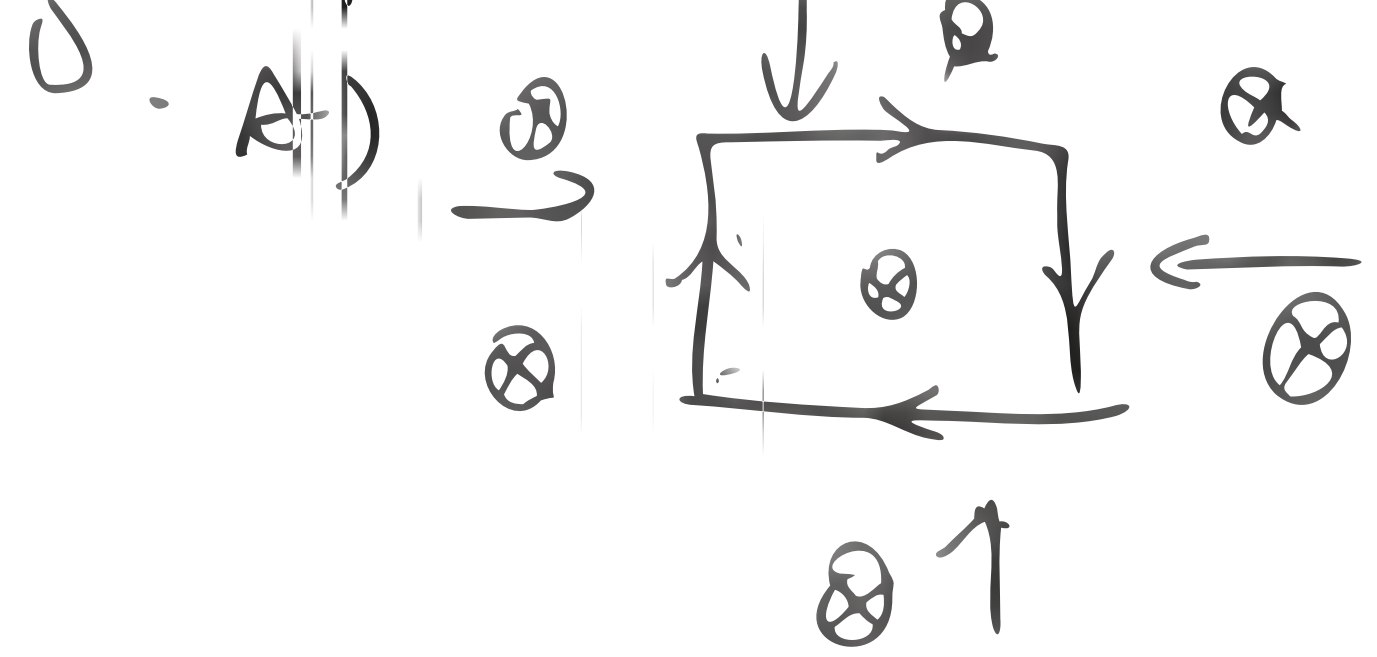


Handwritten: 5/9/2017


Concept Questions



We assume the magnetic field is into the paper
According to the Faraday's theorem, the current is clockwise
The current is such as to oppose the process of its generation
1) the energy came from the hand
2) The energy will almost remain the same but will have some loss.

$$\mathcal{E} = -\frac{d\Phi_B}{dt} \quad I = \frac{\mathcal{E}}{R} \quad R = I^2 R \quad w = I^2 R t$$

2).

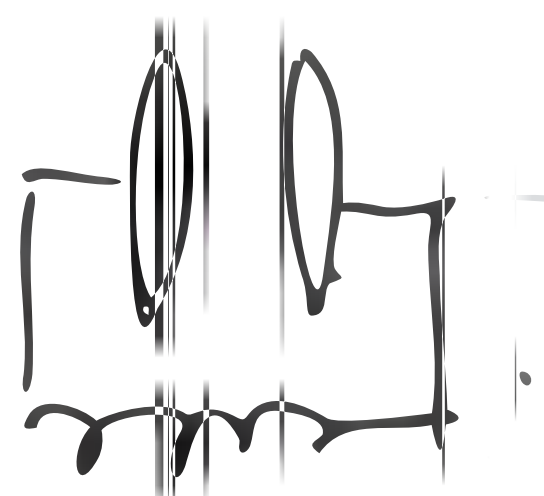


$$C = \frac{\epsilon A}{d} \quad d \downarrow \Rightarrow C \uparrow \quad w = \sqrt{\frac{1}{LC}} \Rightarrow w \downarrow \quad C = \frac{Q}{V_C} \Rightarrow V_C \downarrow$$

$$u = \frac{1}{2} \frac{Q^2}{C^2} \quad u \downarrow \quad u = \frac{1}{2} L I^2 \Rightarrow I \downarrow$$

$$i = -w Q \sin(\omega t + \phi) \quad I \downarrow$$

$$\mathcal{E} = -L \frac{di}{dt} \Rightarrow \mathcal{E} \downarrow$$

\Rightarrow all decreases

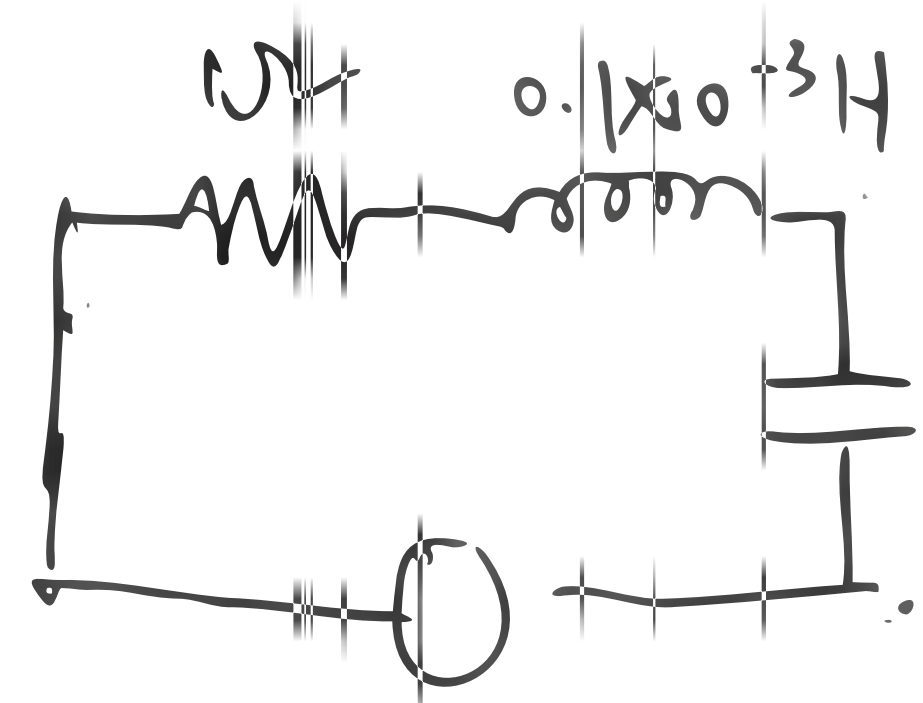

$$f = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(0.1 \times 10^{-3})(1 \times 10^{-3})}} = 503.317 \text{ Hz}$$

$$(b) \left(\frac{R}{2L}\right)^2 - \frac{1}{LC} < 0 \Rightarrow \text{under damped}$$

(c). The energy turned into the heat energy in resistor

$$X_L = \omega L = 2\pi f L = 3 \times 10^{-2} \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = 3.18 \Omega$$

$$X_C > R > X_L \Rightarrow \text{capacitive}$$

Han'abe: 543791023

Essay Question

$$f = 5.5 \times 10^{14} \text{ Hz}$$

$$f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow LC = 0.8 \times 10^{-31} \text{ Hz}^{-2}$$

$$L = \frac{N^2 \mu A}{l}, \mu A = \mu_r \mu_0, N=1, A = \pi r^2 \Rightarrow L = \frac{\mu_r \mu_0 N^2 r^2}{2\pi r^2 \cdot d}$$

Calculation.

$$\textcircled{a} \quad \mathcal{E} = -N \frac{\Delta \Phi}{\Delta t}$$

$$\mathcal{E} = -N \Delta \frac{\Delta B}{\Delta t} = \frac{-1 \times \pi \times (2485 \times 10^3)^2 \times (0.60 \times 10^{-6})}{365 \times 24 \times 60 \times 60} = 21 \times 10^{-6} \text{ V}$$

$$\textcircled{b} \quad B = \frac{\mu_0 I}{2\pi r} \Rightarrow I = \frac{B \cdot 2\pi r}{\mu_0} = \frac{60 \times 10^{-4} \times 2 \times 3485 \times 10^3}{4\pi \times 10^{-7}} = 3.33 \times 10^8 \text{ A}$$

③ counter clock wise \Rightarrow flux is decrease

Calculation.2.



$$I = 10 \cos(2\pi t) \text{ A}, \quad M_1 = M_2 = 1 \times 10^{-3} \text{ H}$$


$$\begin{aligned} 1. \quad \mathcal{E}_2 &= -M_2 \frac{dI}{dt} = -(1 \times 10^{-3}) \times (-10 \sin(2\pi t)) \\ &= 20 \times 10^{-3} \pi \sin(2\pi t) \text{ V} \end{aligned}$$

$$\begin{aligned} 2. \quad R &= 1 \Omega, \quad \mathcal{E}_1 = -M_1 \frac{dI}{dt} \Rightarrow \int dI = - \int \frac{\mathcal{E}_1 dt}{M_1} = - \frac{1}{M_1} \int 10 \cos(2\pi t) dt \\ &= - \frac{5 \times 10^3}{\pi} \sin(2\pi t) \text{ A} \end{aligned}$$

$$3. \quad P = V \cdot I = 100 \text{ W}$$

$$P_2 = V \cdot I = 20 \times 10^{-3} \times \pi \times \frac{5 \times 10^3}{\pi} = 100 \text{ W}$$

$P_1 = P_2 \Rightarrow$ the same

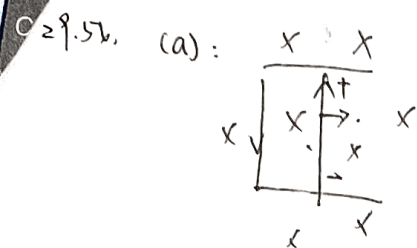


$$\Rightarrow I = \frac{\varepsilon - BIl}{R} = \frac{12V - 2.47 \times 1 \times 0.36m}{-5\Omega} \Rightarrow I = 2.0A$$

$$a = \frac{F}{m} = \frac{BIl \sin 90^\circ}{m} \Rightarrow v \cdot m = \varepsilon \cdot (Bl \cdot \frac{\varepsilon}{R}) - v \cdot \frac{B^2 l^2}{R}$$

$$\Rightarrow v = \frac{13.9}{14} (1 - e^{-\frac{t}{\tau}}) = 0.160t$$

(b). After the switch closed $v=0$ $I = \varepsilon/R = 2.4A$ $F = I l B = 2.07N$ $a = \frac{F}{m} = 2.3 m/s^2$

(c). When $v = 2 m/s$ $a = 2 m/s^2$

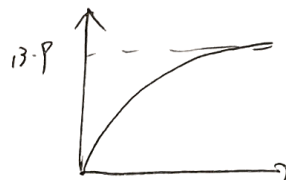

(d). $V_t = \frac{\varepsilon}{Bl} = 13.9 m/s$

30.45

$U_B = \frac{B^2}{2\mu_0} = 6.4 \times 10^4 J/m^3$ $U_B = U_B \cdot V$
 $K = U_B = \frac{1}{2} m v^2 \Rightarrow \frac{1}{2} \rho V v^2 = U_B \cdot V \Rightarrow v = \sqrt{\frac{2U_B}{\rho}} = 1 \times 10^4 m/s$


30.52.

(a) $i_1 + i_2 + i_3 = 0$
 $i_1 \cdot R_1 + i_2 \cdot R_2 = 48$ (*)
 $-i_2 \cdot R_2 + L \frac{di_3}{dt} = 0$
 (b). Steady: $i_2 = 0$ $i_1 = i_3 = \frac{48}{8} = 6A$

(c) According to (*) $i_2 = \frac{\varepsilon - i_3 R_1}{R_1 + R_2}$ $i_3 = \frac{\varepsilon}{R_1} (1 - e^{-\frac{R_1 R_2 t}{L(R_1 + R_2)}})$

(d). $t = \frac{L(R_1 + R_2)}{R_1 R_2} \ln 2 = 0.04s$

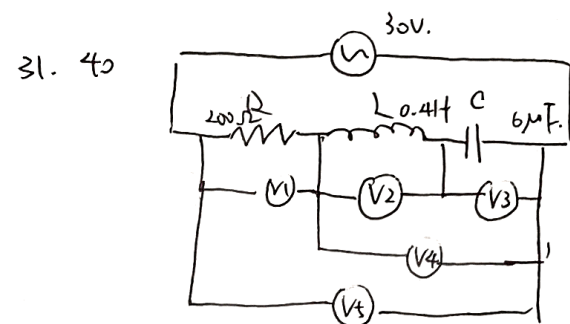e) $i_2 = \frac{\varepsilon - i_3 R_1}{R_1 + R_2} = 1.71A$ $i_1 = i_3 + i_2 = 4.71A$



$U_{rms} = \frac{V}{\sqrt{2}} = 21.2V$
 $\omega = 1000 rad/s \Rightarrow X_L = \omega L = 80\Omega$
 $X_C = \frac{1}{\omega C} = 833\Omega$ $Z = \sqrt{R^2 + (X_L - X_C)^2} = 779\Omega$
 $I_{rms} = \frac{U_{rms}}{Z} = 0.0272A$ $V_1 = R \cdot I_{rms} = 5.44V$


$V_2 = X_L \cdot I_{rms} = 2.18V$ $V_3 = I_{rms} \cdot X_C = 22.7V$

$V_4 = \frac{V_1 - V_3}{\sqrt{2}} = 20.5V$ $V_5 = U_{rms} = 21.2V$

(b). $\omega = 1000 rad/s$ $X_L = \omega L = 400\Omega$ $X_C = \frac{1}{\omega C} = 167\Omega$
 $Z = \sqrt{R^2 + (X_L - X_C)^2} = 307\Omega$ $I_{rms} = \frac{V_{rms}}{Z} = 0.0691A$
 $V_1 = R \cdot I_{rms} = 13.8V$ $V_2 = I_{rms} \cdot X_L = 27.6V$ $V_3 = I_{rms} \cdot X_C = 11.5V$
 $V_4 = |V_2 - V_3| = 16.1V$ $V_5 = U_{rms} = 21.2V$

Han y. bei 54375/122



31.50.

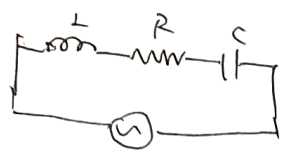


According to 21.49.

(a) $V_L = I \omega L = \frac{V_{WL}}{\sqrt{R^2 + [\omega L - \frac{1}{\omega C}]^2}}$
 (b) $V_C = \frac{I}{\omega C} = \frac{V_{WC}}{\omega C \sqrt{R^2 + [\omega L - \frac{1}{\omega C}]^2}}$

(c).

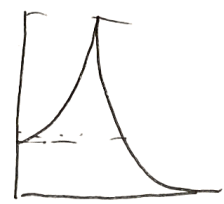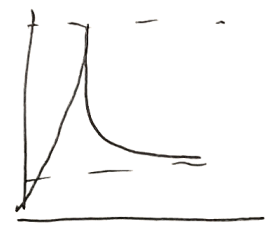

31.62

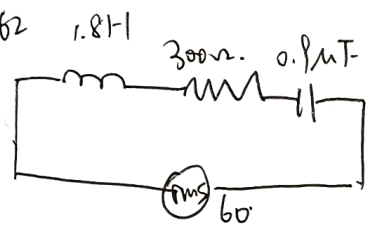

(a) $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1.8H)(9 \times 10^{-7}F)}} = 786 \text{ rad/s}$
 (b) $Z = \sqrt{(300\Omega)^2 + (\omega_0 L - \frac{1}{\omega_0 C})^2} = 300\Omega$

$I_{rms} = \frac{V_{rms}}{Z} = 0.2 \text{ A}$

(c) $I = \frac{4V_{rms}^2}{I^2} = \frac{4V_{rms}^2}{I^2}$

$\omega^2 L^2 + \omega^2 \frac{1}{C^2} - \frac{2L}{C} + R^2 - \frac{4V_{rms}^2}{I_{rms}^2} = 0 \Rightarrow (\omega^2)^2 L^2 + \omega^2 (R - \frac{2L}{C} - \frac{4V_{rms}^2}{I_{rms}^2}) + \frac{1}{C^2} = 0$

$\Rightarrow \omega^2 = 8.9 \times 10^5 / 4.28 \times 10^5$

$\Rightarrow \omega = 943 \text{ rad/s} / 654 \text{ rad/s}$

i) $R = 300\Omega$ $I_{rms} = 0.2 \text{ A}$

$|\omega_1 - \omega_2| = 28 \text{ rad/s}$

ii) $R = 30\Omega$ $I_{rms} = 2 \text{ A}$

$|\omega_1 - \omega_2| = 28 \text{ rad/s}$

iii) $R = 3\Omega$ $I_{rms} = 20 \text{ A}$

$|\omega_1 - \omega_2| = 3 \text{ rad/s}$